



Digital Logic

Lecture 8

2nd Stage

Computer Science Department

Faculty of Science

Soran University


Topics covered

- Multiplexers
- The methods for implementing a circuit using multiplexers.
 - Karnaugh Map Method
 - Algebraic Manipulation
- Logic Expression From Multiplexers

Multiplexers


The multiplexer is a combinational logic circuit designed to switch one of several input lines to a single common output line.

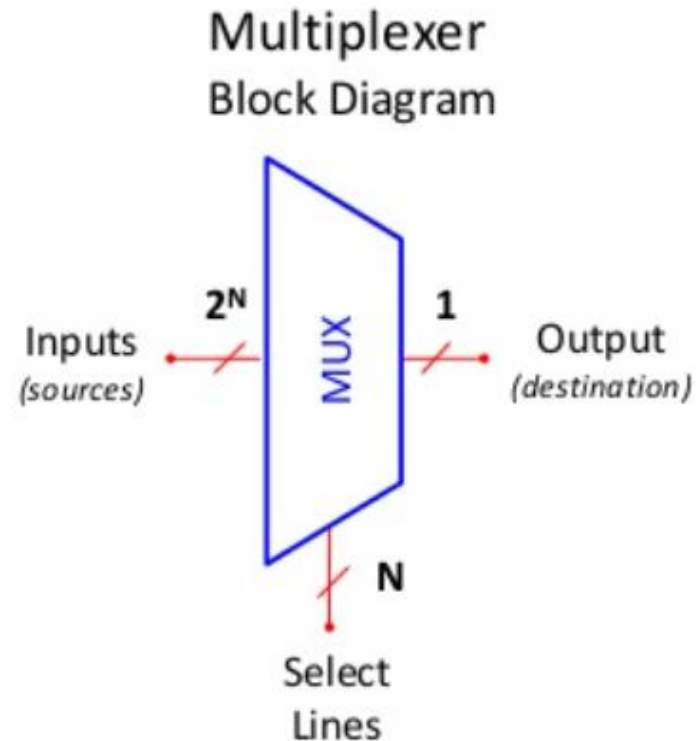- The *multiplexer*, shortened to “**MUX**” or “**MPX**”.
- In digital electronics, multiplexers are also known as **data selectors** because they can “**select**” each input line.




Multiplexers

Typical Application of a MUX

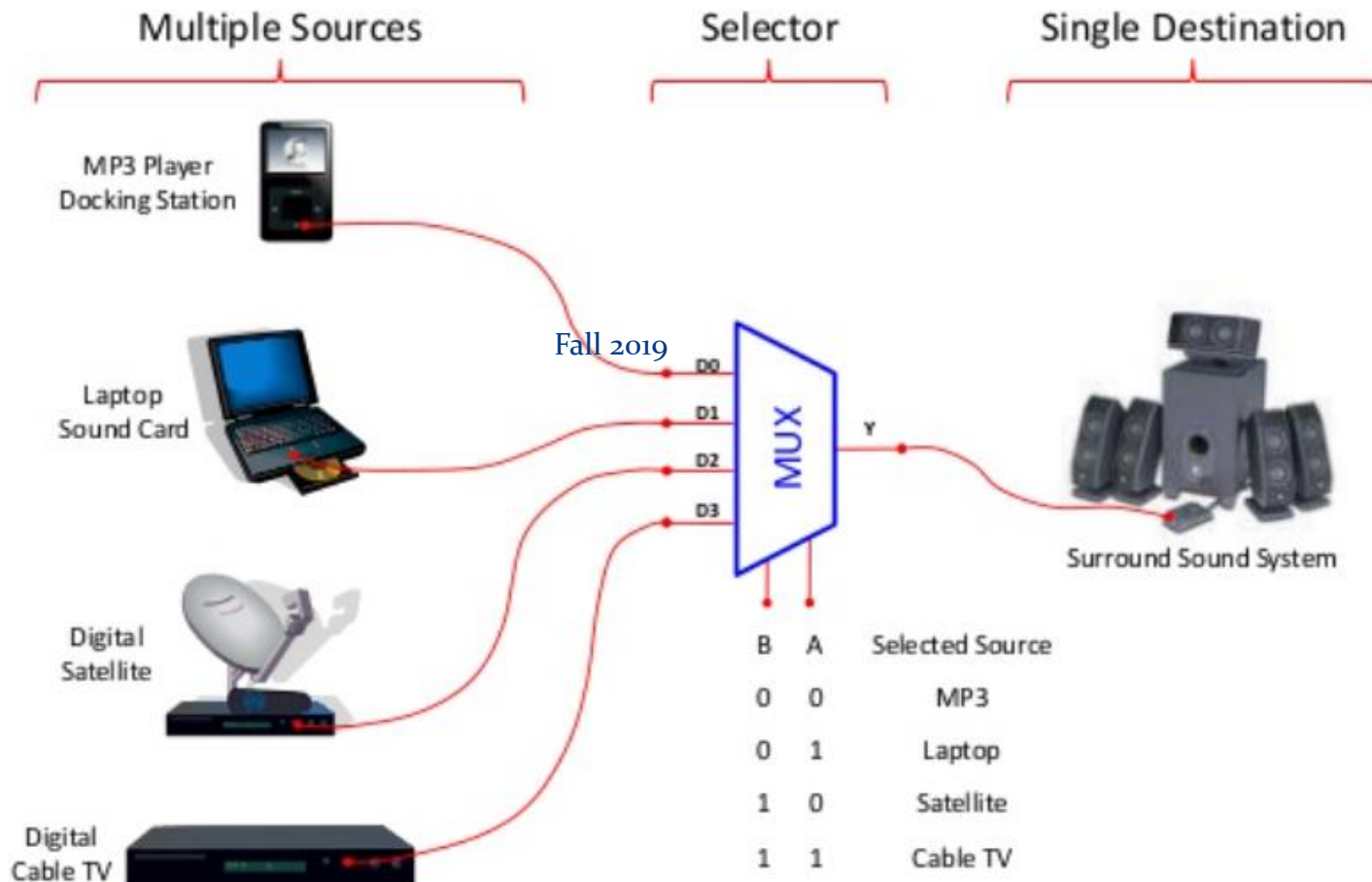

Multiplexers

2 : 1 Multiplexer

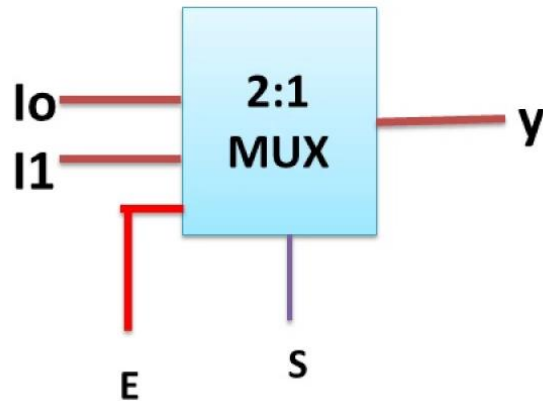


E	S	Y
0	X	0
1	0	I_0
1	1	I_1

$$Y = E.S'.I_0 + E.S.I_1$$

$$Y = E (S'.I_0 + S.I_1)$$


Multiplexers

4 : 1 Multiplexer

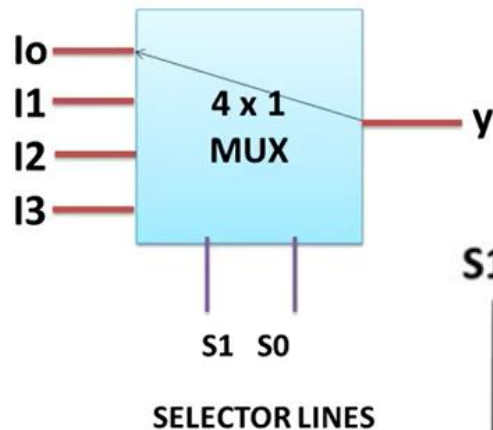


$$Y = S_1'S_0'I_0 + S_1'S_0I_1 + S_1S_0'I_2 + S_1S_0I_3$$

S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

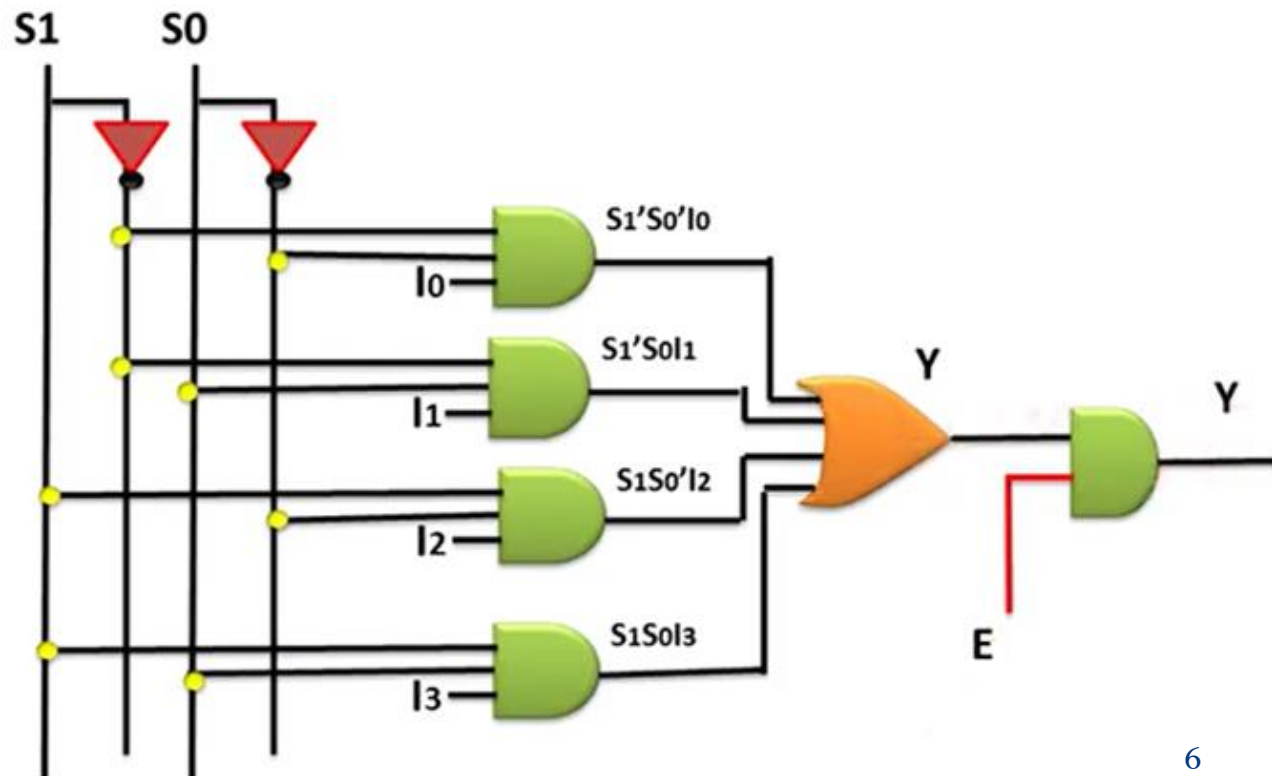

Multiplexers

8 : 1 Multiplexer

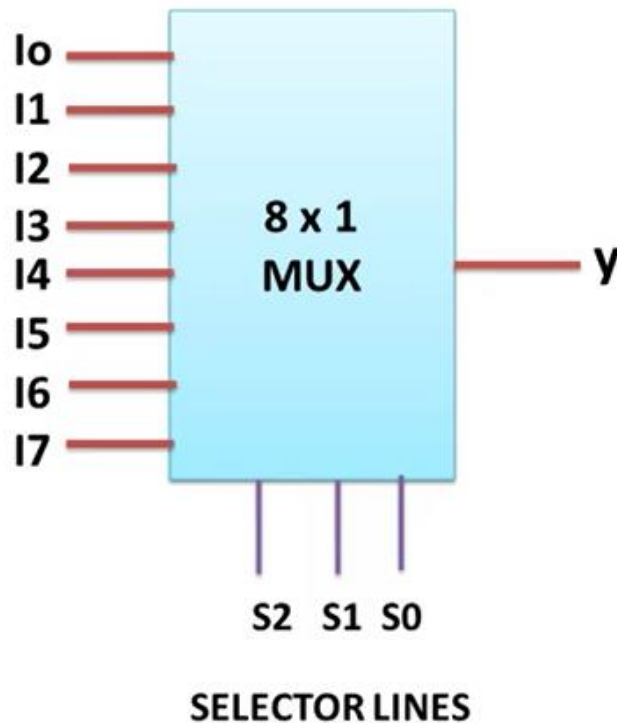


S ₂	S ₁	S ₀	Y
0	0	0	I ₀
0	0	1	I ₁
0	1	0	I ₂
0	1	1	I ₃
1	0	0	I ₄
1	0	1	I ₅
1	1	0	I ₆
1	1	1	I ₇

$$Y = S_2'S_1'S_0'I_0 + S_2'S_1'S_0I_1 + S_2'S_1S_0'I_2 + S_2'S_1S_0I_3 + S_2S_1'S_0'I_4 + S_2S_1'S_0I_5 + S_2S_1S_0'I_6 + S_2S_1S_0I_7$$

Multiplexers
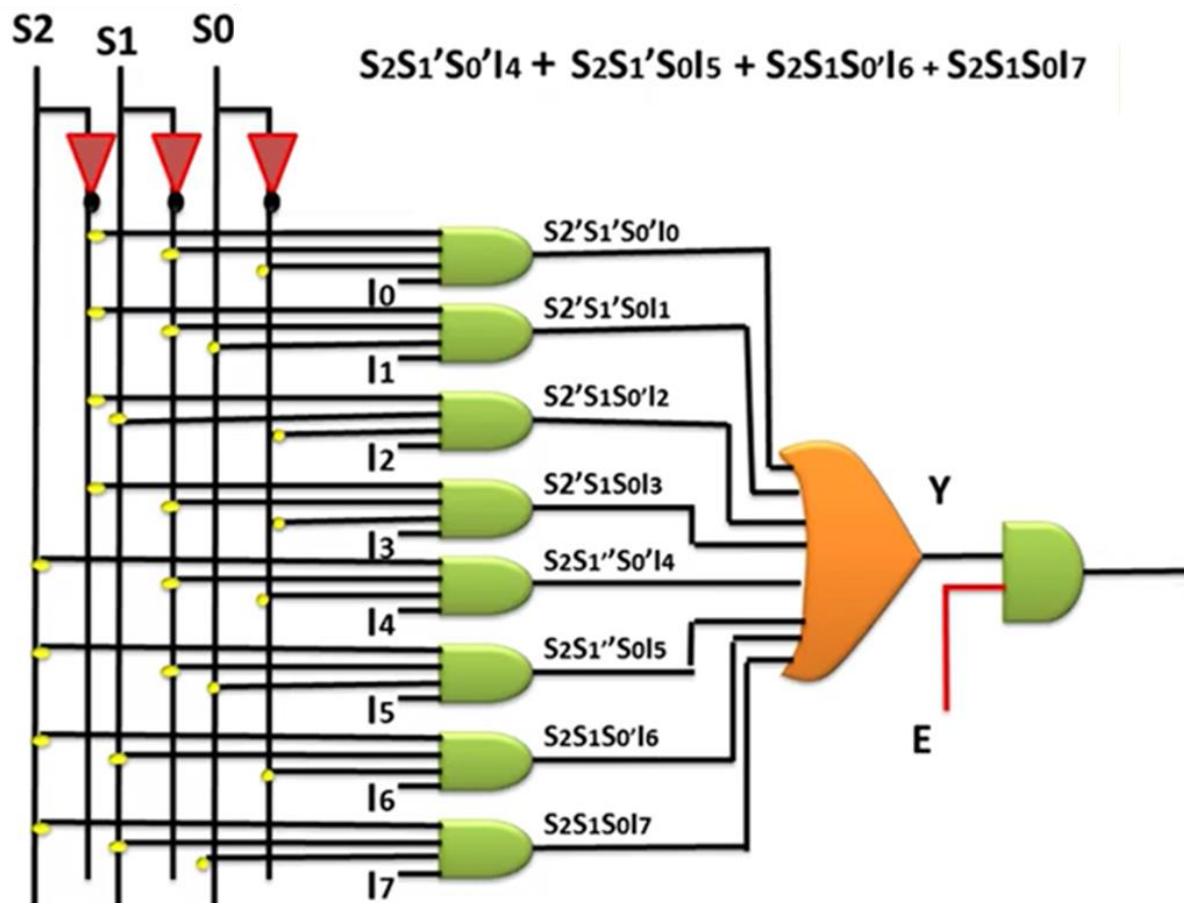
$$Y = S_2'S_1'S_0'I_0 + S_2'S_1'S_0'I_1 + S_2'S_1S_0'I_2 + S_2'S_1S_0'I_3 + S_2S_1'S_0'I_4 + S_2S_1'S_0'I_5 + S_2S_1S_0'I_6 + S_2S_1S_0'I_7$$



Karnaugh Map **Method for** **Implementation of** **Multiplexers**

Multiplexers using Karnaugh Map

Example 1: Consider the function: $f(A,B,C) = \bar{A}B + BC + \bar{A}C$
the data variable has been suggested although any variable can be chosen as the data variable and the other two as the select variables.


Solution:

Suppose one were to take **A** as the data variable. and **B, C** to be the select variables. The corresponding Karnaugh map is then:

A ← Data Variable

BC	0	1	
00	0	0	$\bar{B}\bar{C} = 0$
01	1	0	$\bar{B}C = \bar{A}$
11	1	1	$BC = 1$
10	1	0	$B\bar{C} = \bar{A}$

↑
Select Variables

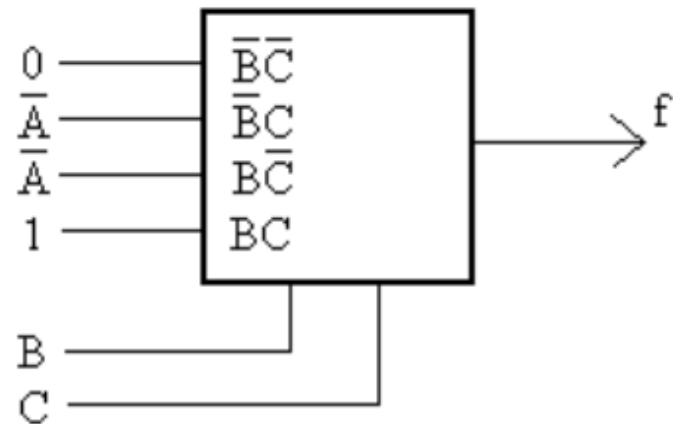

Multiplexers using Karnaugh Map



Example 2: Design multiplexer implementations for the following functions using the **Karnaugh map method**.

- For the first problem, use **A** as the **data variable** and **B,C** as the **select variables**.
- For the second problem, use **C** as the **data variable** and **A,B** as the **select variables**.

$$Z = f(A,B,C) = \overline{A}\overline{B}\overline{C} + \overline{A}B + A\overline{B}\overline{C} + AC$$

$$Z = f(A,B,C) = \overline{A}B + \overline{B}C + BC + A\overline{B}\overline{C}$$

Multiplexers using Karnaugh Map

Solution 1:


Using **A** as the **data variable** and **B,C** as the **select variables**:

A ← Data Variable

BC	0	1	
00	1	0	$\overline{B}\overline{C} = \overline{A}$
01	0	1	$\overline{B}C = A$
11	1	1	$BC = 1$
10	1	1	$B\overline{C} = 1$

↑
Select Variables
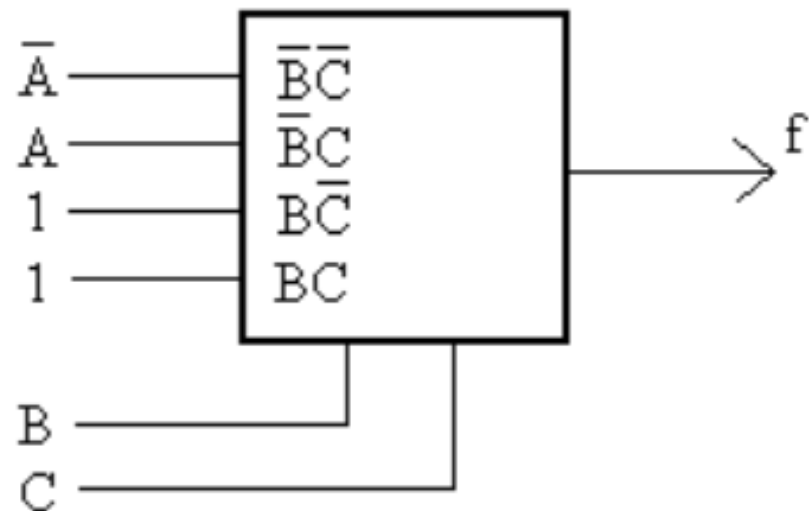
$$Z = f(A,B,C) = \overline{A}\overline{B}\overline{C} + \overline{A}B + A\overline{B}\overline{C} + AC$$



Multiplexers using Karnaugh Map

Solution 2:


Using **C** as the **data variable** and **A,B** as the **select variables**:

C ← Data Variable

AB	0	1	
00	0	1	$\bar{A}\bar{B} = C$
01	1	1	$\bar{A}B = 1$
11	0	1	$AB = C$
10	1	1	$A\bar{B} = 1$

↑
Select Variables
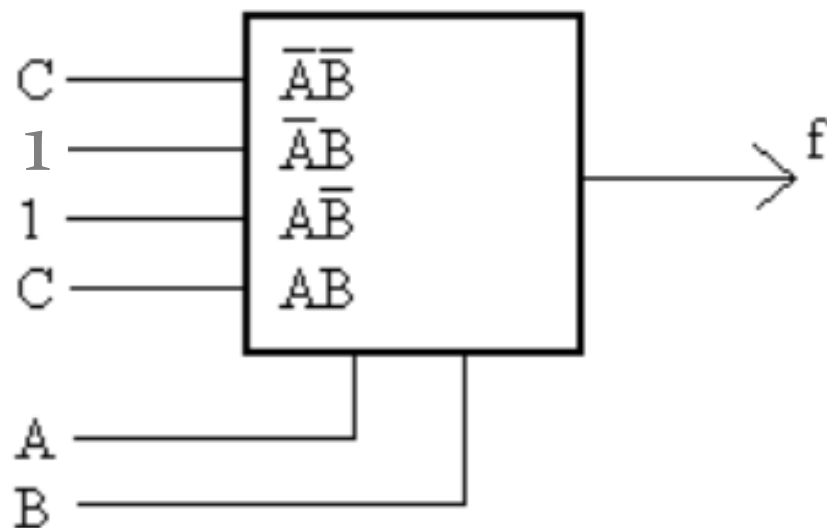
$$Z = f(A,B,C) = \bar{A}\bar{B} + \bar{B}C + BC + A\bar{B}\bar{C}$$



Algebraic Method for Implementation of Multiplexers

Multiplexers using Algebraic Methods

Example 1: Consider the function: $f(A,B,C) = \bar{A}B + BC + \bar{A}C$

Expanding to canonical sum of products form:


$$f(A,B,C) = \bar{A}B(C + \bar{C}) + BC(A + \bar{A}) + \bar{A}C(B + \bar{B})$$

$$= \bar{A}BC + \bar{A}B\bar{C} + ABC + \bar{A}BC + \bar{A}BC + \bar{A}BC$$

$$= \bar{A}BC + \bar{A}B\bar{C} + \bar{A}BC + ABC$$

$$= \bar{A}BC + \bar{A}B(C + \bar{C}) + ABC$$
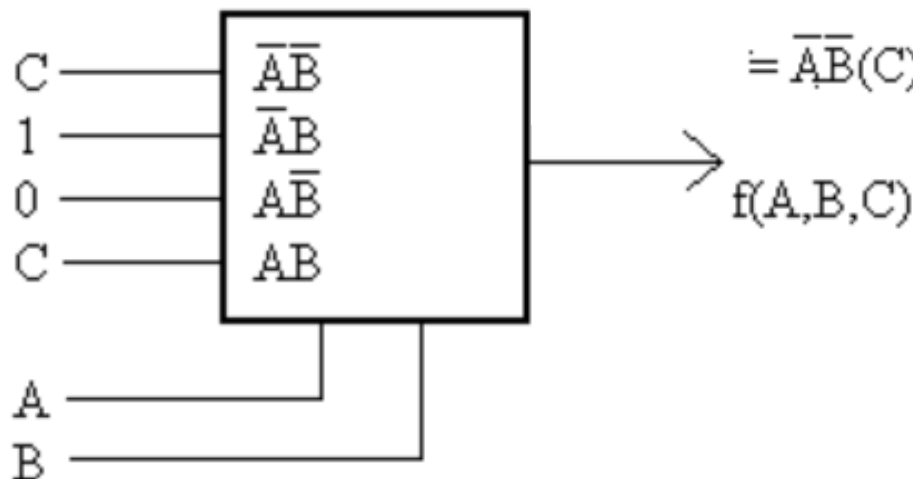
$$= \bar{A}\bar{B}(C) + \bar{A}B(1) + A\bar{B}(0) + AB(C)$$




Multiplexers using Algebraic Methods

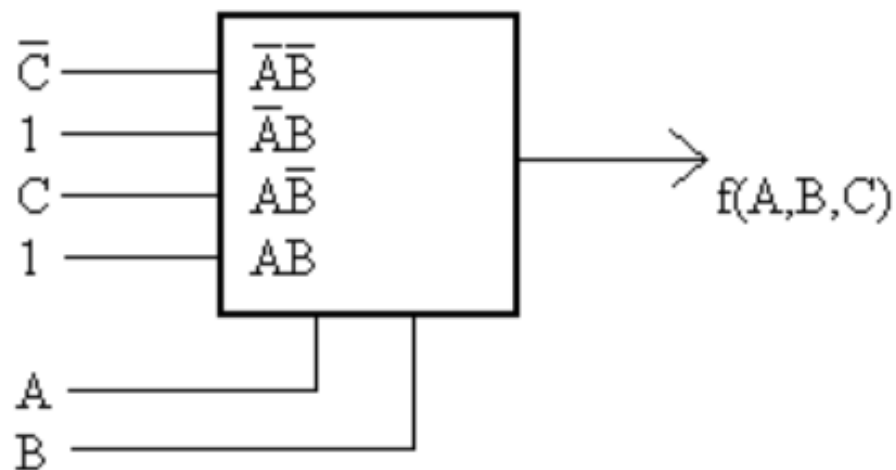Example 2: Consider the function below:

Expanding to sum of products form

$$\begin{aligned} F(A,B, C) &= \bar{A}\bar{B}\bar{C} + \bar{A}B(C + \bar{C}) + A\bar{B}\bar{C} + AC(B + \bar{B}) \\ &= \bar{A}\bar{B}\bar{C} + \bar{A}BC + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC + A\bar{B}C \\ &= \bar{A}\bar{B}(\bar{C}) + \bar{A}B(1) + AB(1) + A\bar{B}(C) \end{aligned}$$




Multiplexers using Algebraic Methods

Example 3:

Expanding to sum of products form:

$$\begin{aligned}
 F(A,B,C) &= \bar{A}B(C + \bar{C}) + \bar{B}C(A + \bar{A}) + BC(A + \bar{A}) + A\bar{B}\bar{C} \\
 &= \cancel{\bar{A}BC} + \bar{A}B\bar{C} + \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C} + A\bar{B}C + \cancel{A\bar{B}\bar{C}} + A\bar{B}\bar{C} \\
 &= \bar{A}B\bar{C} + \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} + A\bar{B}C \\
 &= \bar{A}B\bar{C} + \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C} + AC(B + \bar{B}) \\
 &= \bar{A}B\bar{C} + \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C} + AC(1)
 \end{aligned}$$

What is
wrong?

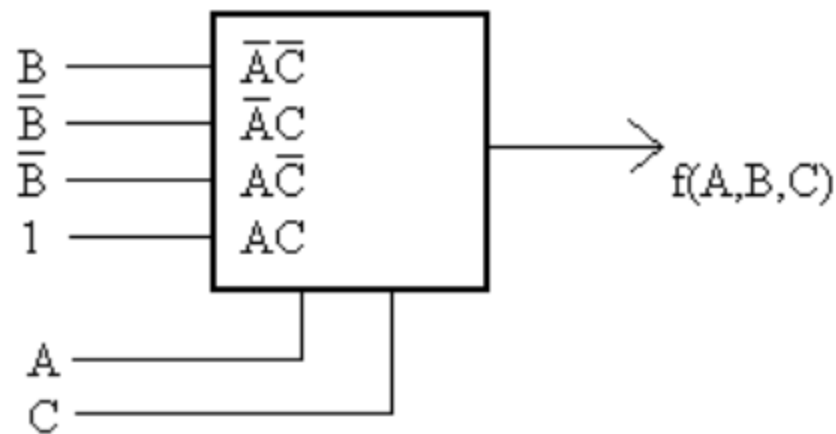


Implementing Boolean Functions with a Multiplexer

$$F(x,y,z) = \sum m(1, 2, 6, 7)$$

X	Y	Z	F	
0	0	0	0	$F = Z$
0	0	1	1	
0	1	0	1	$F = \bar{Z}$
0	1	1	0	
1	0	0	0	$F = 0$
1	0	1	0	
1	1	0	1	$F = 1$
1	1	1	1	

(a) Truth table

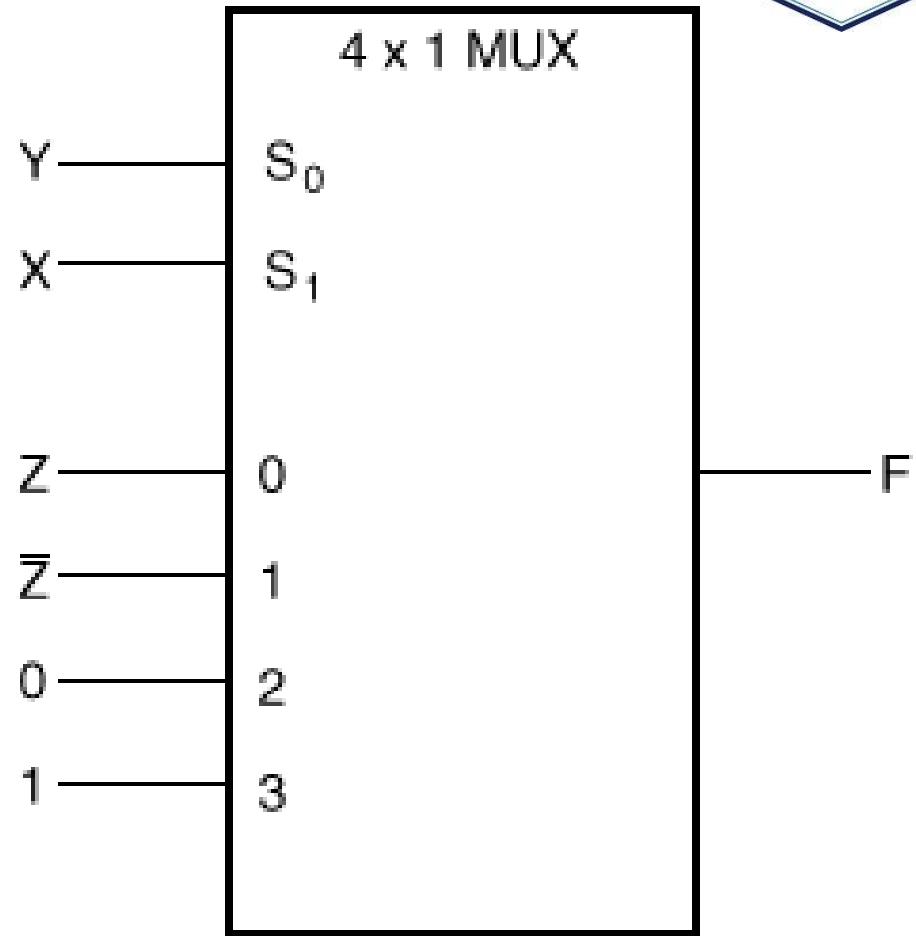


(b) Multiplexer implementation

Implementing Boolean Functions with a Multiplexer

$$F(A,B,C,D) = \sum m(1,3,4,11,12, 13, 14, 15)$$

A	B	C	D	F	
0	0	0	0	0	$F = D$
0	0	0	1	1	
0	0	1	0	0	$F = D$
0	0	1	1	1	
0	1	0	0	1	$F = \bar{D}$
0	1	0	1	0	
0	1	1	0	0	$F = 0$
0	1	1	1	0	
1	0	0	0	0	$F = 0$
1	0	0	1	0	
1	0	1	0	0	$F = D$
1	0	1	1	1	
1	1	0	0	1	$F = 1$
1	1	0	1	1	
1	1	1	0	1	$F = 1$
1	1	1	1	1	

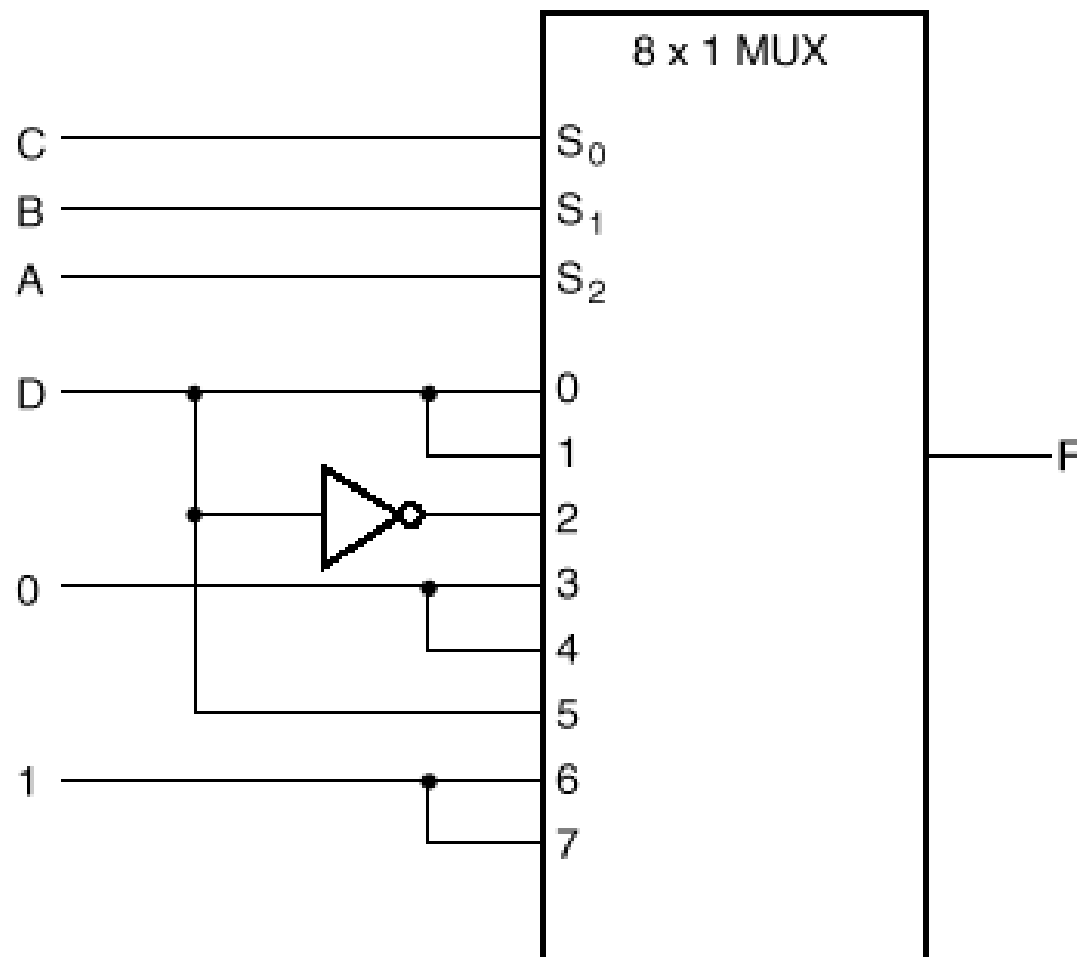

Implementing Boolean Functions with a Multiplexer


Implement the following Boolean function using 4:1 Multiplexer $F(A,B,C) = \sum m(1,3,5,6)$

Minterm	A	B	C	F
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

Truth Table

	D ₀	D ₁	D ₂	D ₃
\bar{A}	0	①	2	③
A	4	⑤	⑥	7
	0	1	A	\bar{A}

Implementation Table

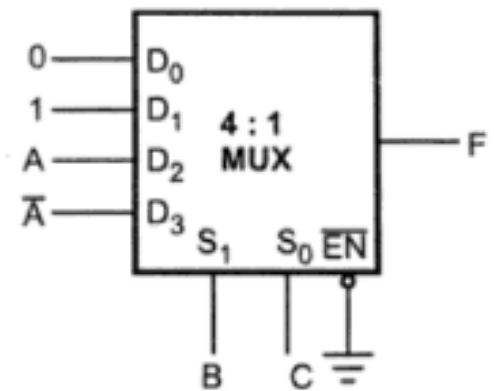


Multiplexer Implementation

Implementing Boolean Functions with a Multiplexer

Implement the following Boolean function using 8:1 Multiplexer
 $F(A,B,C,D) = \sum m(0,1,3,4,8,9,15)$

	D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇
\bar{A}	①	①	2	③	④	5	6	7
A	⑧	⑨	10	11	12	13	14	⑮
	1	1	0	\bar{A}	\bar{A}	0	0	A

Implementation Table

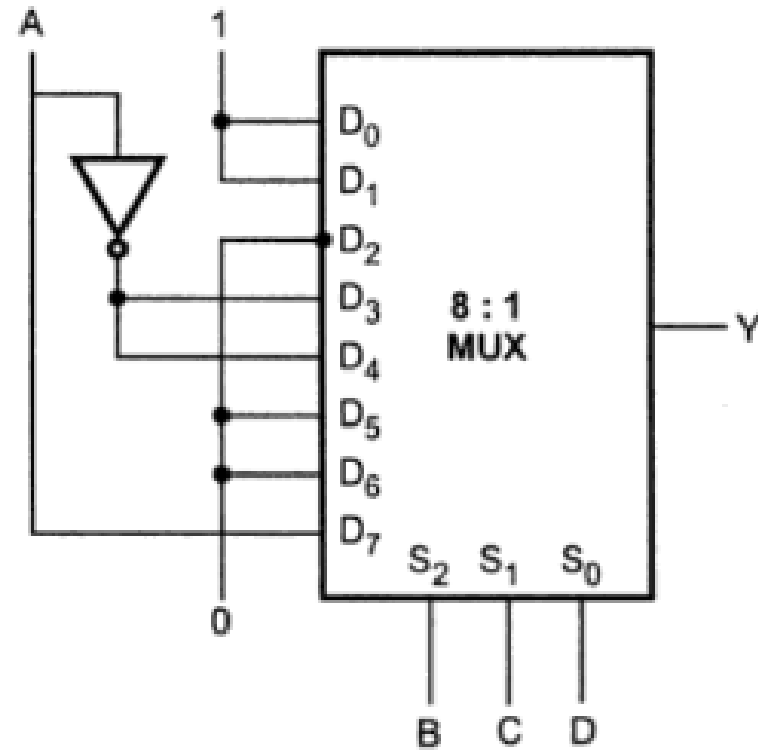


Multiplexer Implementation

Implementing Boolean Functions with a Multiplexer



Implement the following Boolean function using 8:1 Multiplexer
 $F(A,B,C,D) = \sum m(0,2,3,6,8,10,11,12,13,14)$

	D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇
\bar{A}	0	1	2	3	4	5	6	7
A	8	9	10	11	12	13	14	15
	1	0	1	1	A	A	1	0

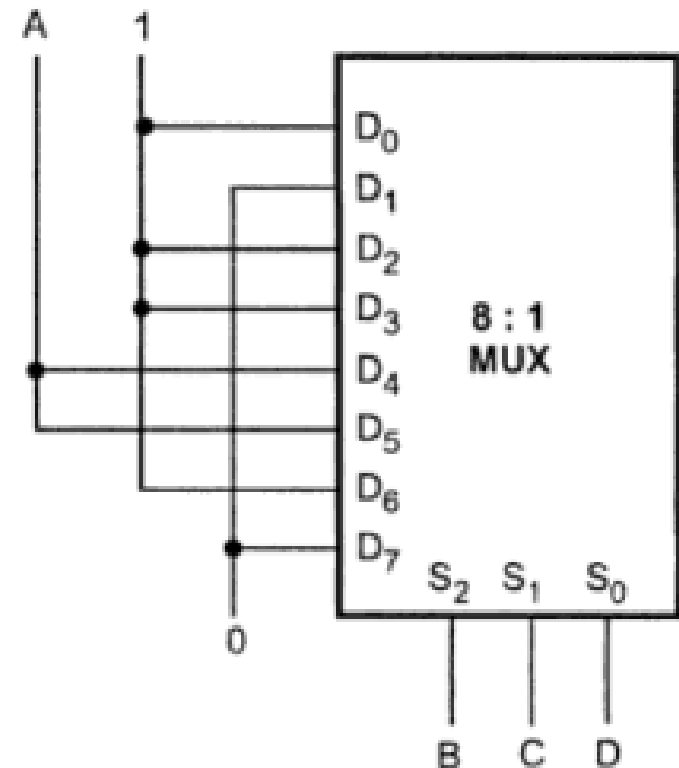


Multiplexer as a Full-Adder

INPUTS			OUTPUTS	
A	B	Cin	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

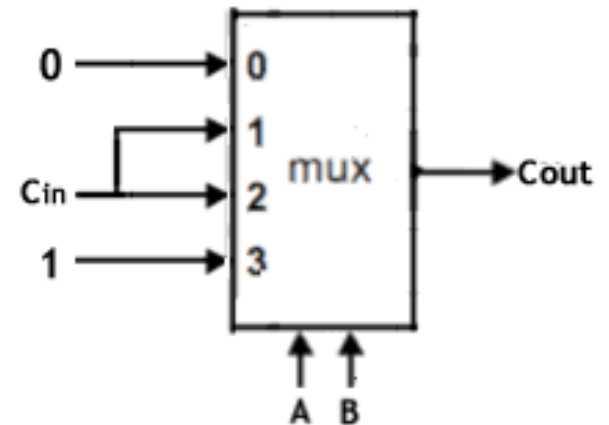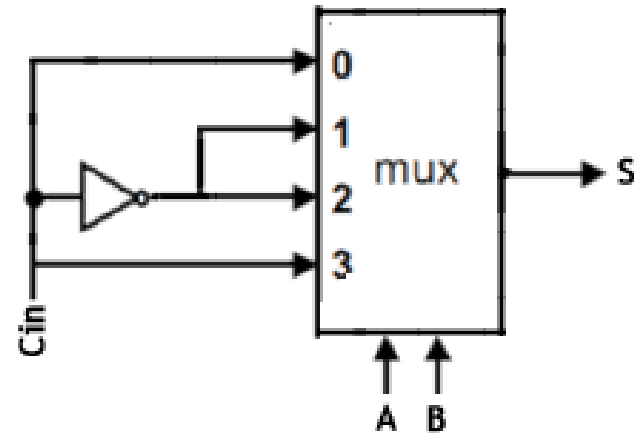

Logic Expression From Multiplexers

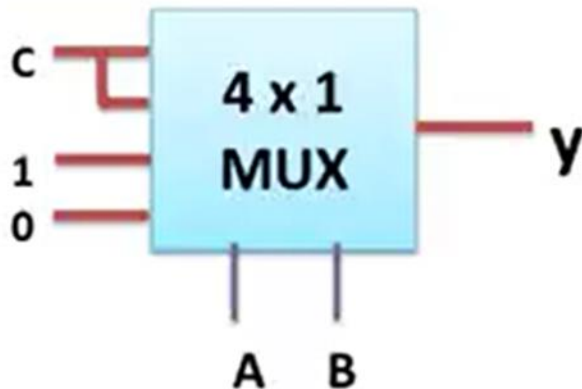

A	B	Y
0	0	I ₀
0	1	I ₁
1	0	I ₂
1	1	I ₃


A	B	Y
0	0	C
0	1	C
1	0	1
1	1	0

$$Y = A'B'C + A'BC + AB'1 + AB0$$

$$Y = A'C(B+B') + AB'$$

$$Y = A'C + AB'$$

Logic Expression From Multiplexers

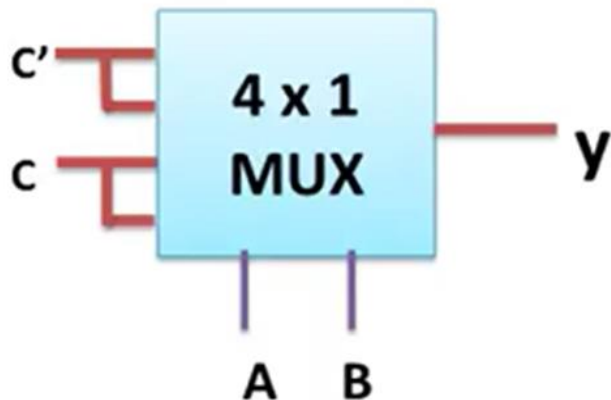

A	B	Y
0	0	l ₀
0	1	l ₁
1	0	l ₂
1	1	l ₃

A	B	Y
0	0	C'
0	1	C'
1	0	C
1	1	C

$$Y = A'C' + AC$$

Try


Implement the following Boolean function using a Multiplexers.

$$F(A,B,C,D) = \sum m(0, 4, 5, 6, 7, 9, 13, 15)$$

- i. Draw the Multiplexer Block diagram
- ii. Draw the Multiplexer using logic gates.
- iii. Fully label all inputs and outputs

Try

Construct the equivalent multiplexer for the following logic diagram, use B as the data variable and A,C as the select variables.

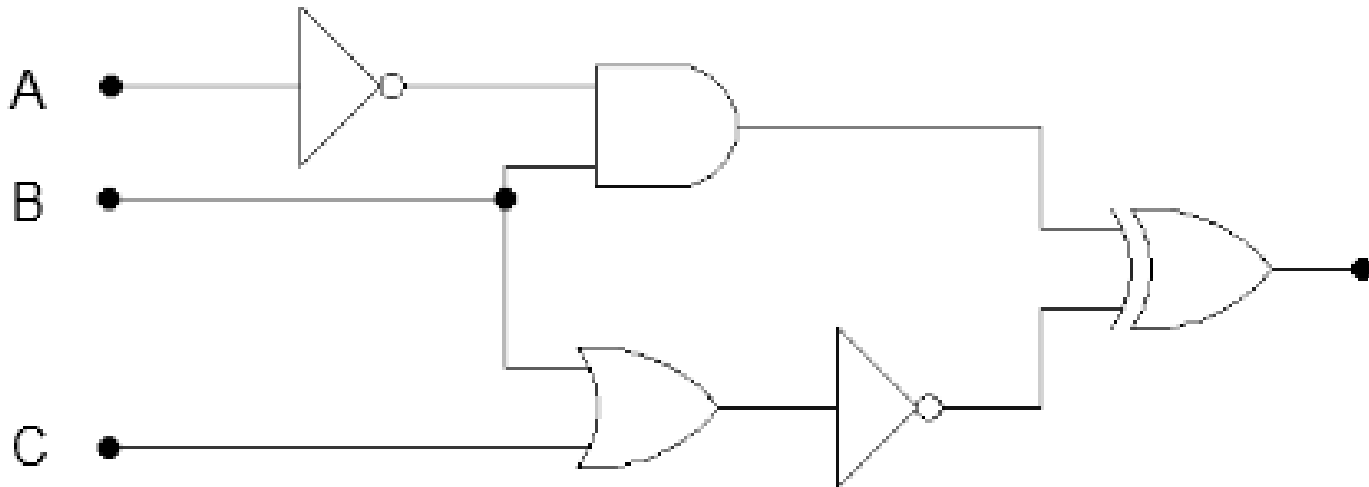

Homework 9



Q1) Implement a full subtractor with two 4:1 multiplexers.

Q2) Implement the following Boolean function with two 4:1 and one 2:1 multiplexers.

$$F(w, x, y, z) = \Pi M(3, 10, 11)$$

Deadline: December 16, 2022 @ 11:59 PM