



Digital Logic

Lecture 9

2nd Stage

Computer Science Department

Faculty of Science

Soran University


Topics covered

DeMultiplexers

- Applications of Demultiplexer
- 1:N DeMultiplexers
 - 1:2 DEMUX
 - 1:4 DEMUX
 - 1:8 DEMUX
 - 1:16 DEMUX

What is a Demultiplexer (DEMUX)?

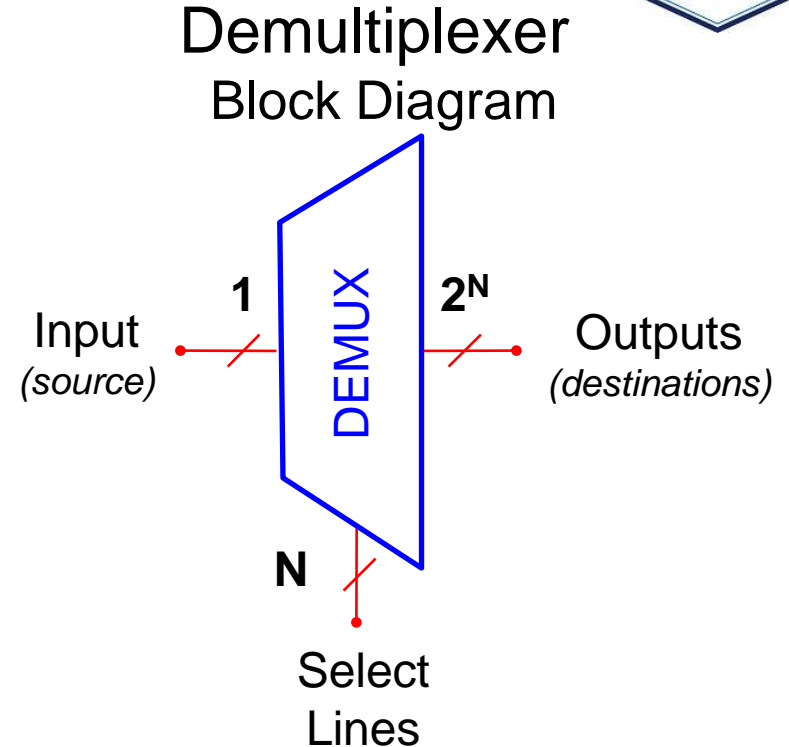- A DEMUX is a digital switch with a single input (source) and a multiple outputs (destinations).
- The select lines determine which output the input is connected to.



What is a Demultiplexer (DEMUX)?

- ✧ Demultiplexer is exactly reverse of multiplexer.
- ✧ Relationship between m & n is given by

$$2^m = n$$

where m = no. of control lines, n = no. of output lines


- ✧ So we can have

1:2 DEMUX; with 1 Select line


1:4 DEMUX; with 2 Select lines

1:8 DEMUX; with 3 Select lines

1:16 DEMUX; with 4 Select lines

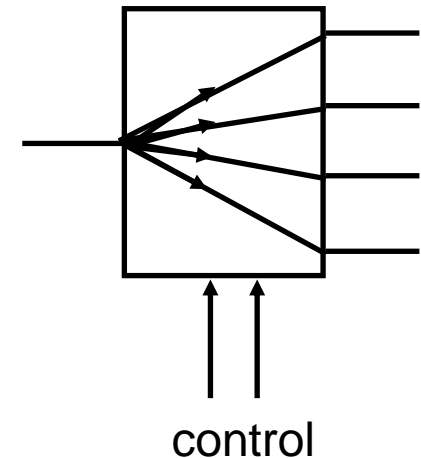


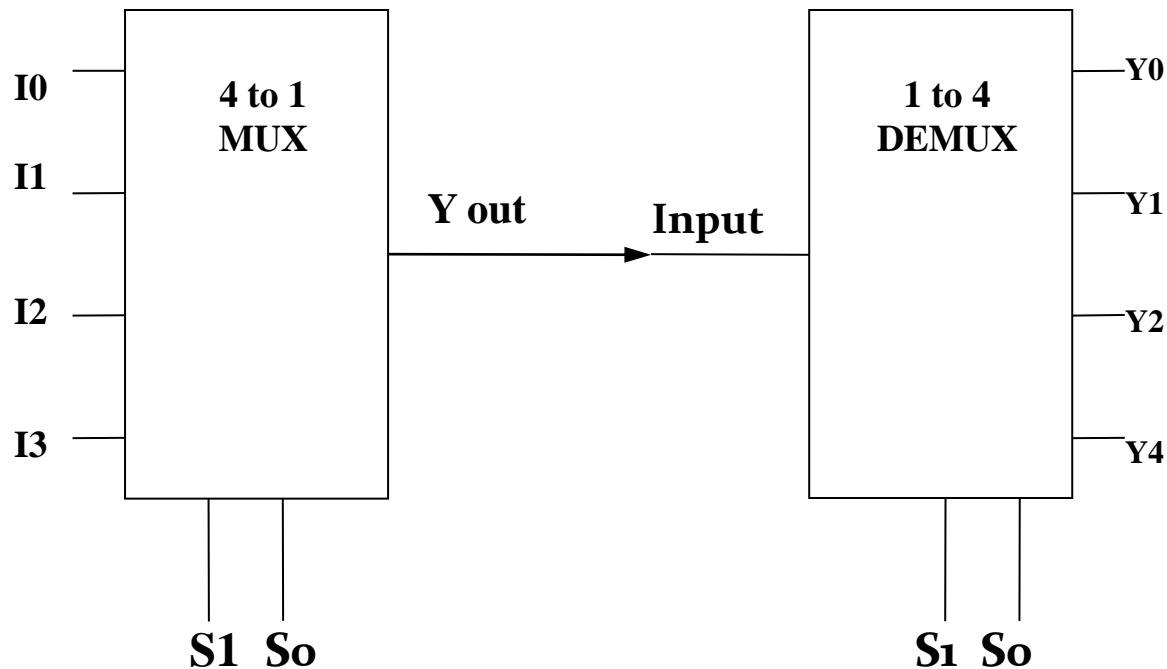Relation between a Multiplexer and a Demultiplexer




Applications of Demultiplexer

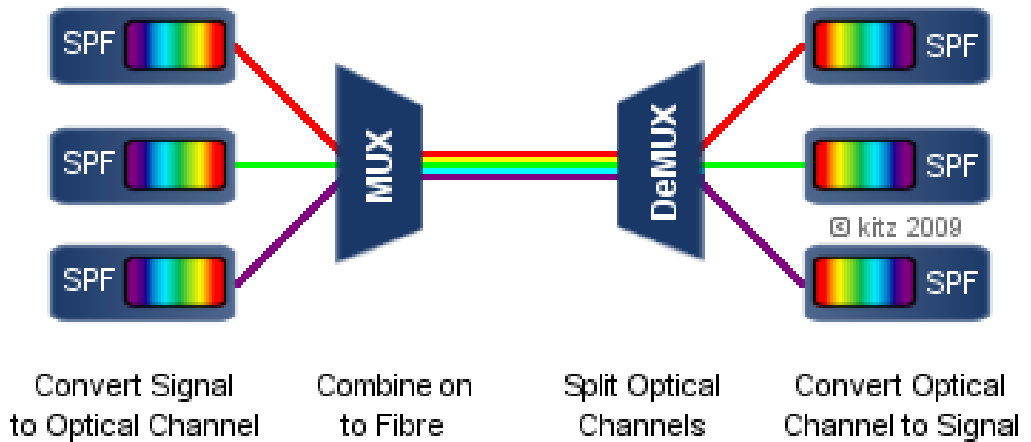- Communication Systems
- Arithmetic Logic Unit
- Serial to Parallel Converter



Typical Application of a DEMUX

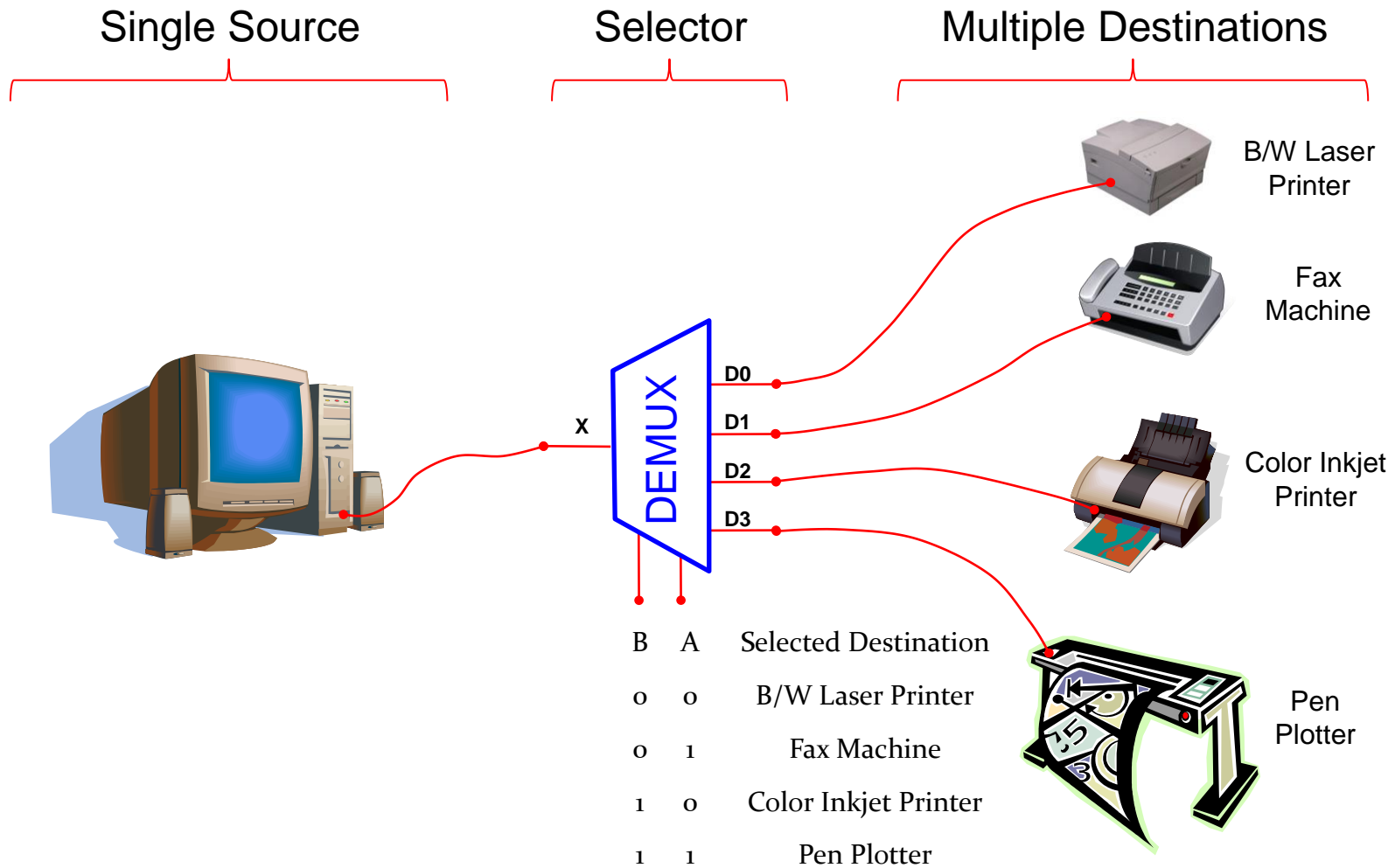


1 to 2 Demultiplexer

1:2 Demultiplexer Truthtable

| S | D ₀ | D ₁ |
|---|----------------|----------------|
| 0 | X | 0 |
| 1 | 0 | X |


1:2 Demultiplexer Graphical Symbol

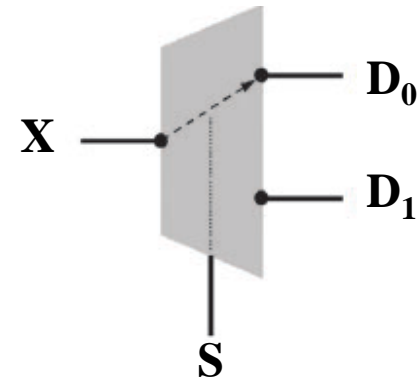

1:2 Demultiplexer Logic Expressions


$$D_0 = S'.X$$

$$D_1 = S.X$$

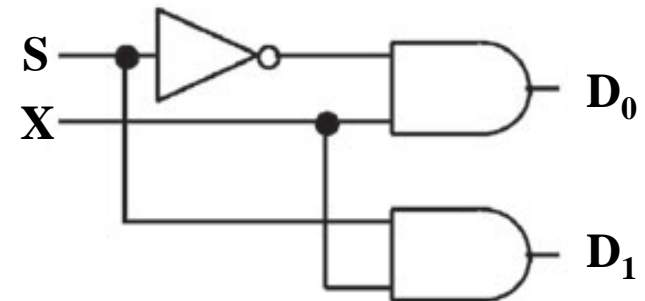

1:2 Demultiplexer Logic Diagram

1 to 4 Demultiplexer

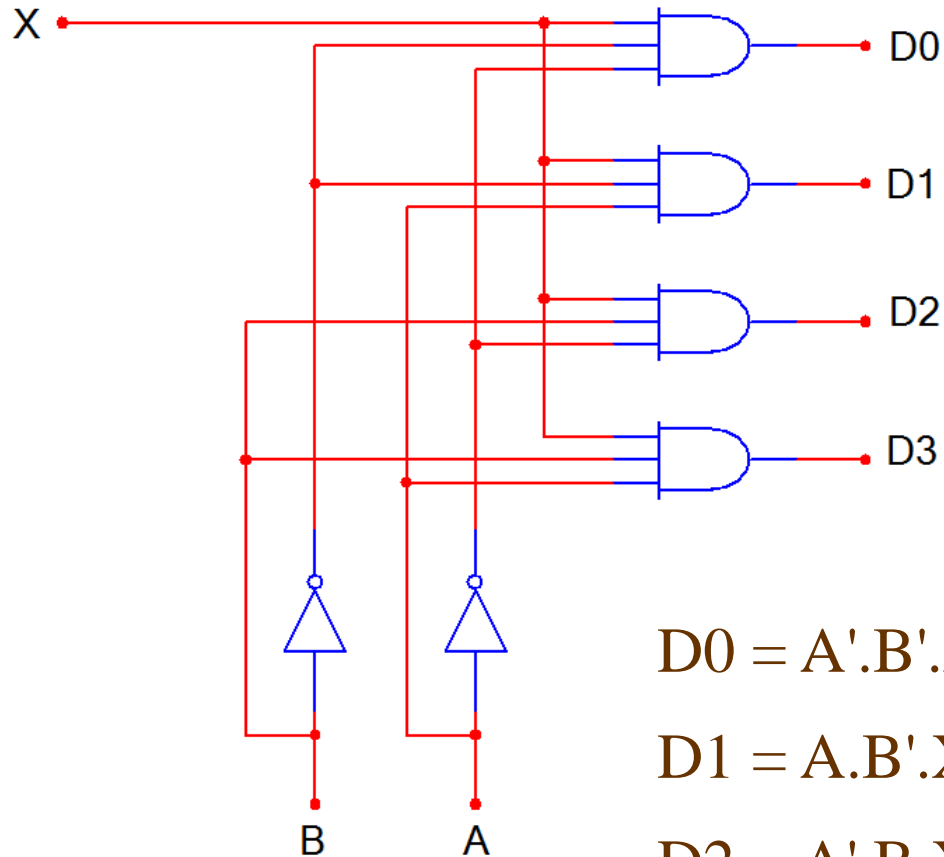


$$D0 = A'.B'.X$$

$$D1 = A.B'.X$$

$$D2 = A'.B.X$$

$$D3 = A.B.X$$

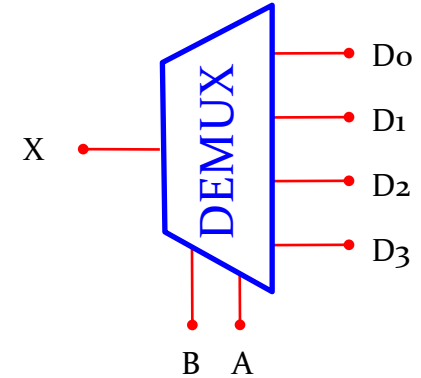

| B | A | D ₀ | D ₁ | D ₂ | D ₃ |
|---|---|----------------|----------------|----------------|----------------|
| 0 | 0 | X | 0 | 0 | 0 |
| 0 | 1 | 0 | X | 0 | 0 |
| 1 | 0 | 0 | 0 | X | 0 |
| 1 | 1 | 0 | 0 | 0 | X |

1 to 8 Demultiplexer

| Data Input | Select Inputs | | | Outputs | | | | | | | |
|------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|
| D | S ₂ | S ₁ | S ₀ | Y ₇ | Y ₆ | Y ₅ | Y ₄ | Y ₃ | Y ₂ | Y ₁ | Y ₀ |
| D | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | D |
| D | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | D | 0 |
| D | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | D | 0 | 0 |
| D | 0 | 1 | 1 | 0 | 0 | 0 | 0 | D | 0 | 0 | 0 |
| D | 1 | 0 | 0 | 0 | 0 | 0 | D | 0 | 0 | 0 | 0 |
| D | 1 | 0 | 1 | 0 | 0 | D | 0 | 0 | 0 | 0 | 0 |
| D | 1 | 1 | 0 | 0 | D | 0 | 0 | 0 | 0 | 0 | 0 |
| D | 1 | 1 | 1 | D | 0 | 0 | 0 | 0 | 0 | 0 | 0 |

1 to 8 De-Multiplexer Truth Table

1 to 8 Demultiplexer

$$Y_0 = D \overline{S_2} \overline{S_1} \overline{S_0}$$

$$Y_1 = D \overline{S_2} \overline{S_1} S_0$$

$$Y_2 = D \overline{S_2} S_1 \overline{S_0}$$


$$Y_3 = D \overline{S_2} S_1 S_0$$

$$Y_4 = D S_2 \overline{S_1} \overline{S_0}$$

$$Y_5 = D S_2 \overline{S_1} S_0$$

$$Y_6 = D S_2 S_1 \overline{S_0}$$

$$Y_7 = D S_2 S_1 S_0$$

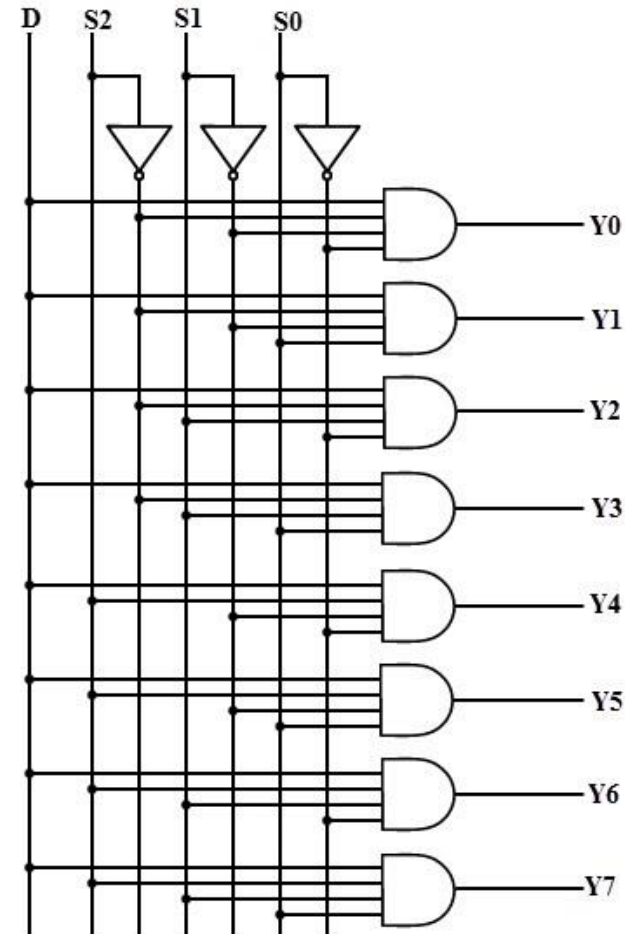


1 to 8 Demultiplexer Logic Expression

1 to 8 Demultiplexer Logic Diagram


1 to 8 Demultiplexer

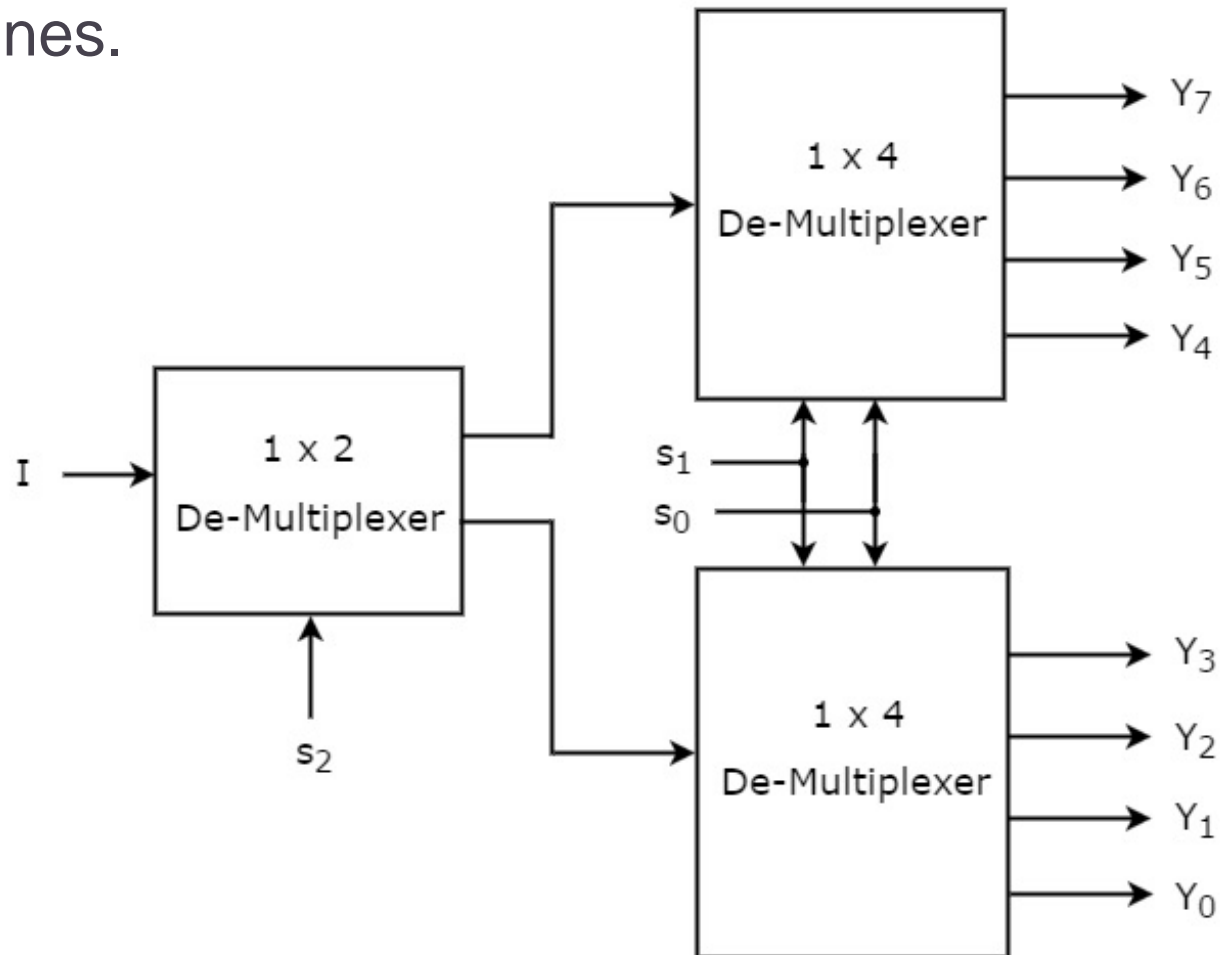A 1 to 8 demultiplexer consists of one input line, 8 output lines and 3 select lines.




1 to 16 Demultiplexer

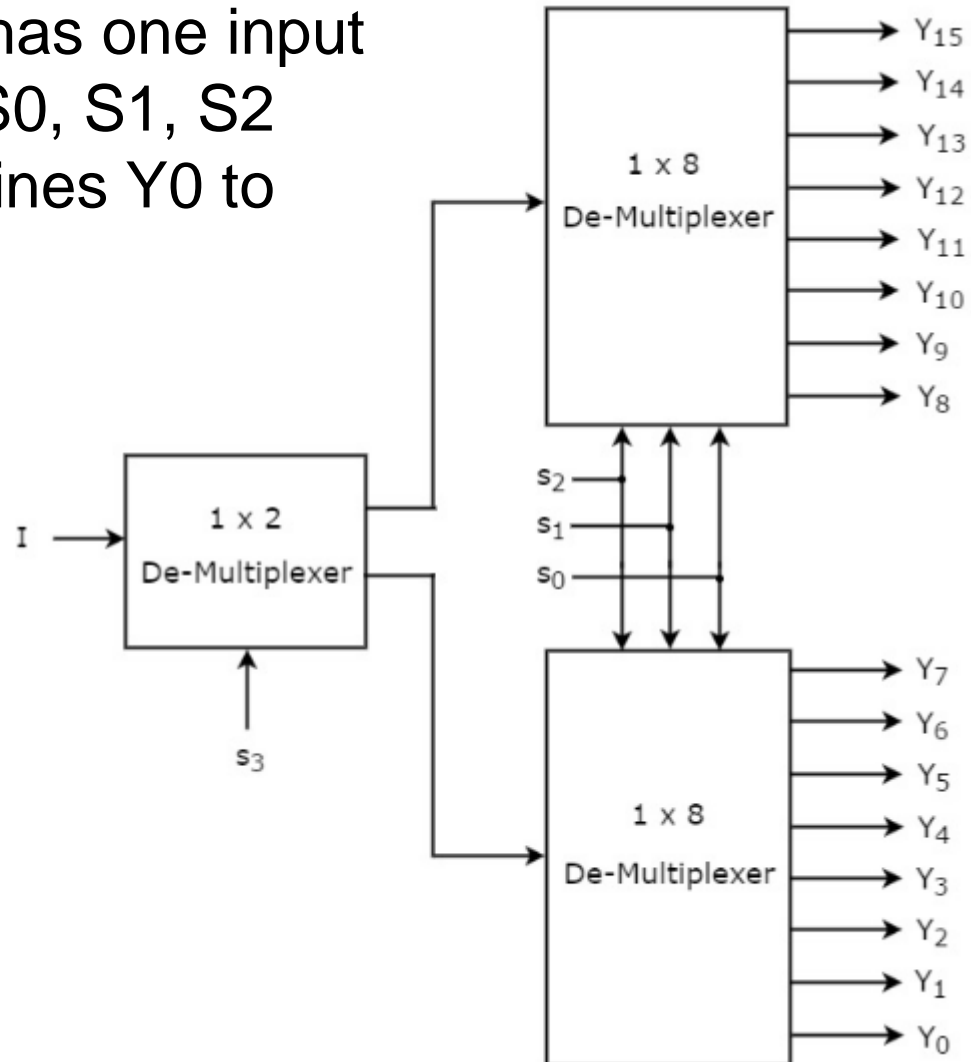
1 to 16 de-multiplexer has one input data, four select lines S_0 , S_1 , S_2 and S_3 and 16 output lines Y_0 to Y_{15} .




2:1 MUX and 1:2 DEMUX Communication

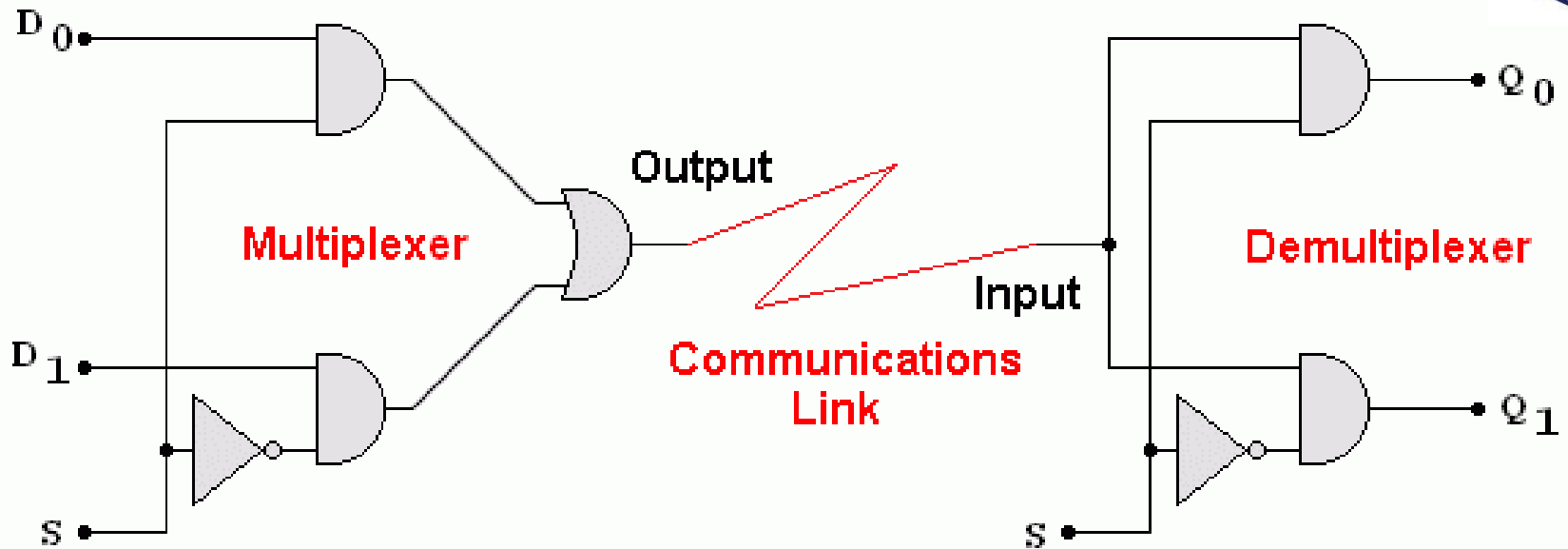

4:1 MUX and 1:4 DEMUX Communication

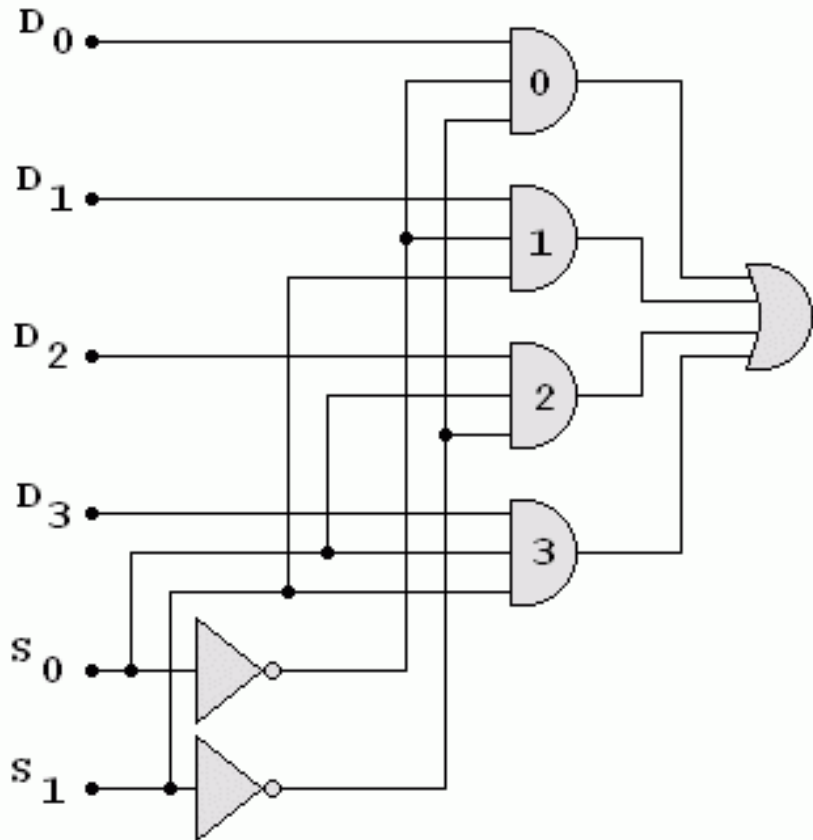

4:1 MUX

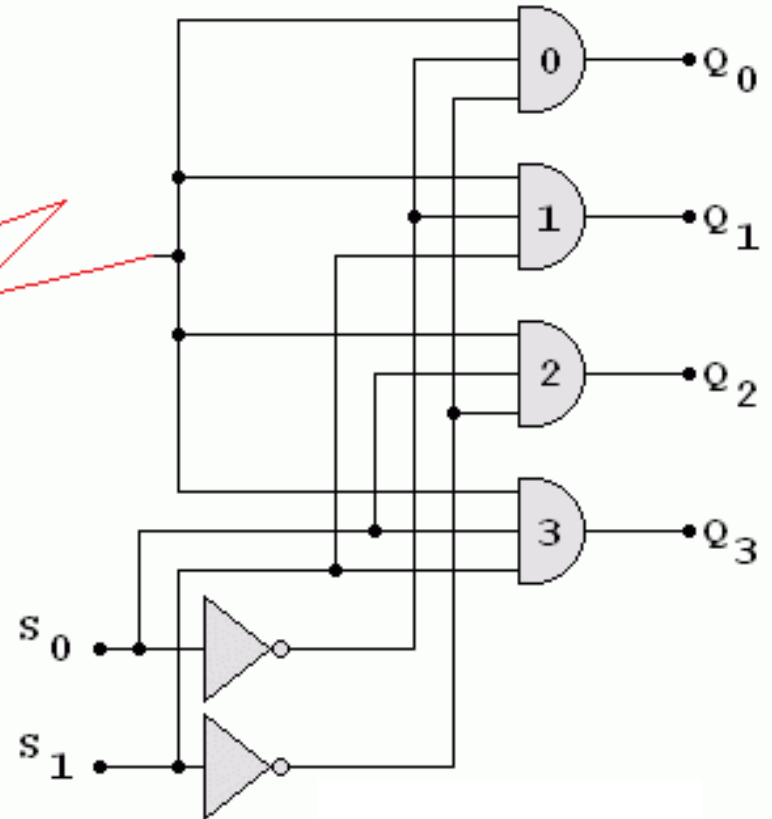

1:4 DEMUX

Try



Q1) Construct a 16:1 multiplexer with 2:1 multiplexers only. Use block diagrams, and logic diagrams

Q2) Construct a 1:16 demultiplexer with 1:2 demultiplexers only. Use block diagrams, and logic diagrams